

5ή Εργαστηριακή Άσκηση

ΥΛΟΠΟΙΗΣΗ ΠΡΑΞΕΩΝ ΓΙΑ ΣΧΕΔΙΑΣΗ ΑΡΙΘΜΟΜΗΧΑΝΗΣ

(Behavioral and Structural VHDL)

Ομάδα LAB20332005

ΧΡΗΣΤΟΣ ΖΗΣΚΑΣ 2014030191
ΠΑΝΑΓΙΩΤΗΣ ΣΑΒΒΑΙΔΗΣ 2013030180

Σκοπός εργαστηριακής άσκησης


Σκοπός της τελευταίας εργαστηριακής άσκησης είναι η εκ-νέου επέκταση της υλοποίησης του εργαστηρίου 3- έχει διαμορφωθεί το σχέδιο για την αναγνώριση των πράξεων- με τον σχεδιασμό και την εκτέλεση των πράξεων ώστε να τελειοποιηθεί το μοντέλο της αριθμομηχανής. Η σχεδίαση επικεντρώνεται στην αντιπροσώπευση του κάθε κουμπιού στην εκάστοτε πράξη όταν το σύστημα βρίσκεται στα διάφορα mode. Η κάθε πράξη αποκωδικοποιείται από μια μηχανή πεπερασμένων καταστάσεων ενώ για την ολοκλήρωση της κάθε πράξης απαιτείται κάποιο υποσύστημα που διαμορφώνει το data path(πρόσθετης- αφαιρέτης, καταχωρητές , αναγνώριση της υπερχείλισης στον προσθέτη- αφαιρέτη) και ολοκληρώνει τη μοντελοποίηση της στοίβας με τη σύνδεση συνδυαστικών κυκλωμάτων .

Προεργασία


Η προετοιμασία του κυκλώματος απαιτεί :

- ◆ Το block diagram της συνολικής σχεδίασης – συμπεριλαμβάνει τις μηχανές πεπερασμένων καταστάσεων που κατευθύνουν την εκτέλεση των κουμπιών και των δομών που πραγματοποιούν τις πράξεις και το συγκροτημένο σχήμα της μνήμης.
- ◆ Επέκταση της διεπαφής του κυκλώματος με τα 7-segment display για την απεικόνιση των διαφόρων αποτελεσμάτων σε κάθε διασταύρωση του κυκλώματος
- ◆ Διαγράμματα των νέων μηχανών πεπερασμένων καταστάσεων (3 νέες fsm – αφορούν τις εκάστοτε πράξεις . Το add και το sub συγχρονίζονται σε μια μηχανή
- ◆ Κατασκευή κατάλληλων test για την αναγνώριση του σωστού σχεδιασμού του συστήματος στην προσομοίωση .

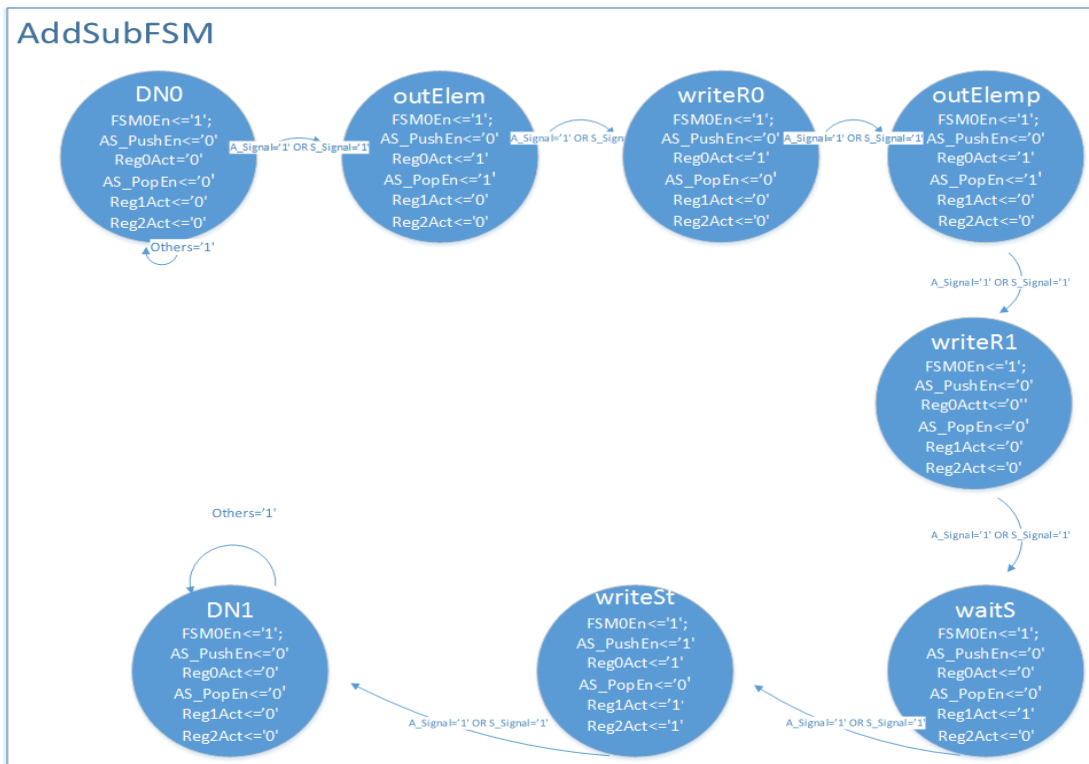
Μηχανή Πεπερασμένων Καταστάσεων για την εκάστοτε πράξη Add-Sub(ASFSM)



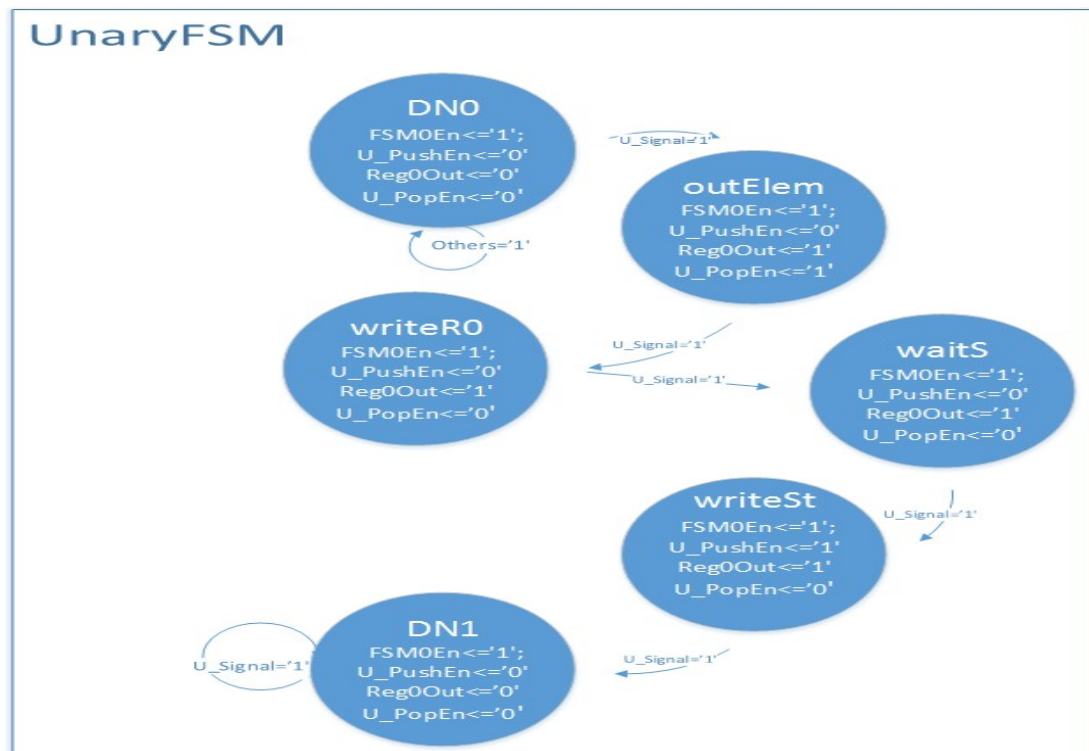
Μηχανή Πεπερασμένων Καταστάσεων για την πράξη UnarySub(UFSM)



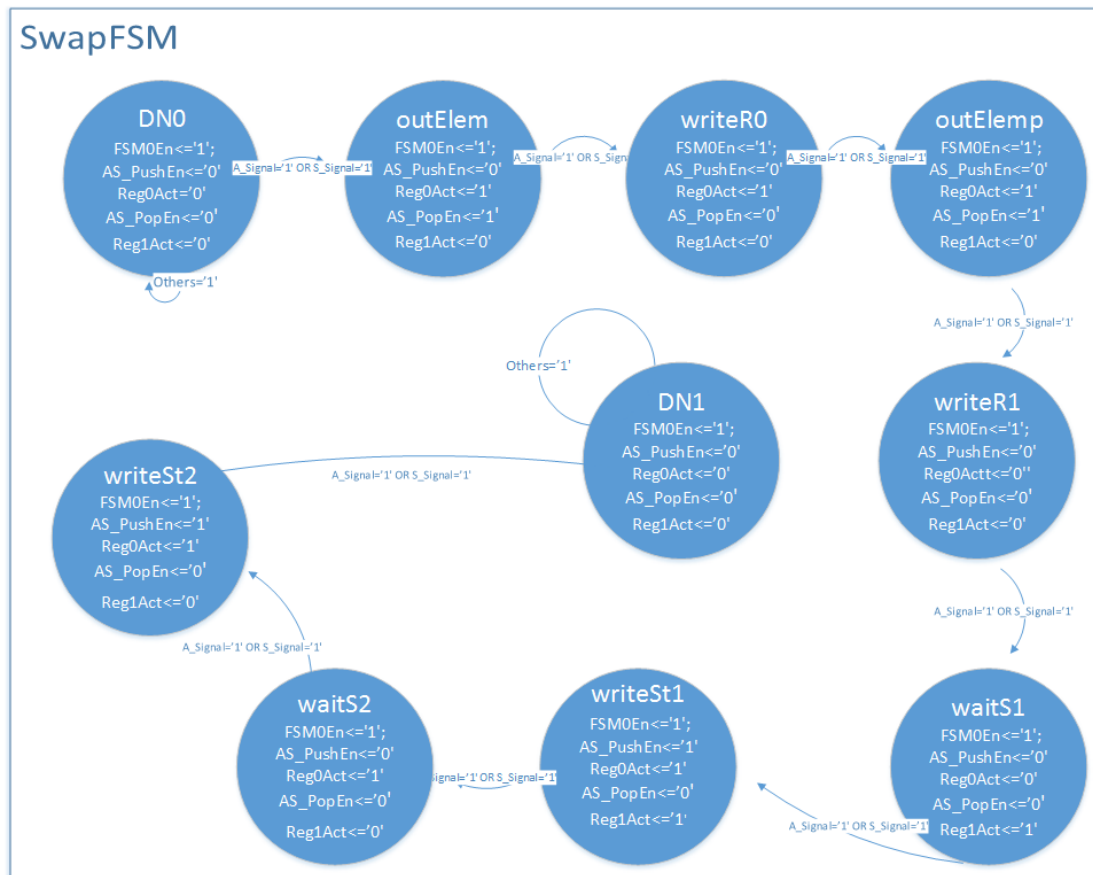
Μηχανή Πεπερασμένων Καταστάσεων για την πράξη Swap (SwapFSM)




Υλοποίηση Ολοκληρωμένου κυκλώματος Στοιβάς (Stack)

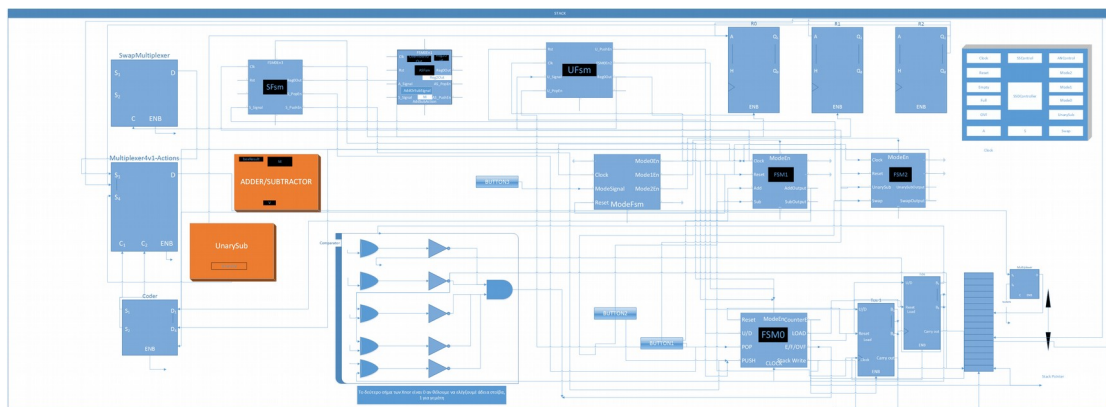

Υλοποίηση 7-segment Display

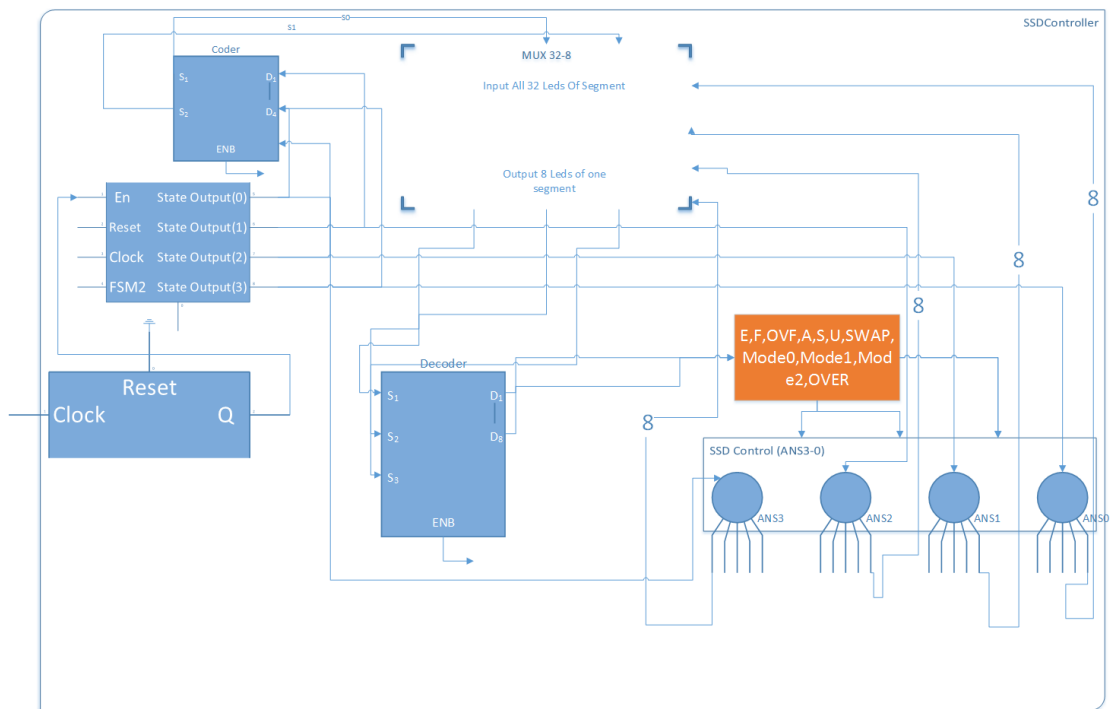

Υλοποίηση δομής προσθαφαιρέτη

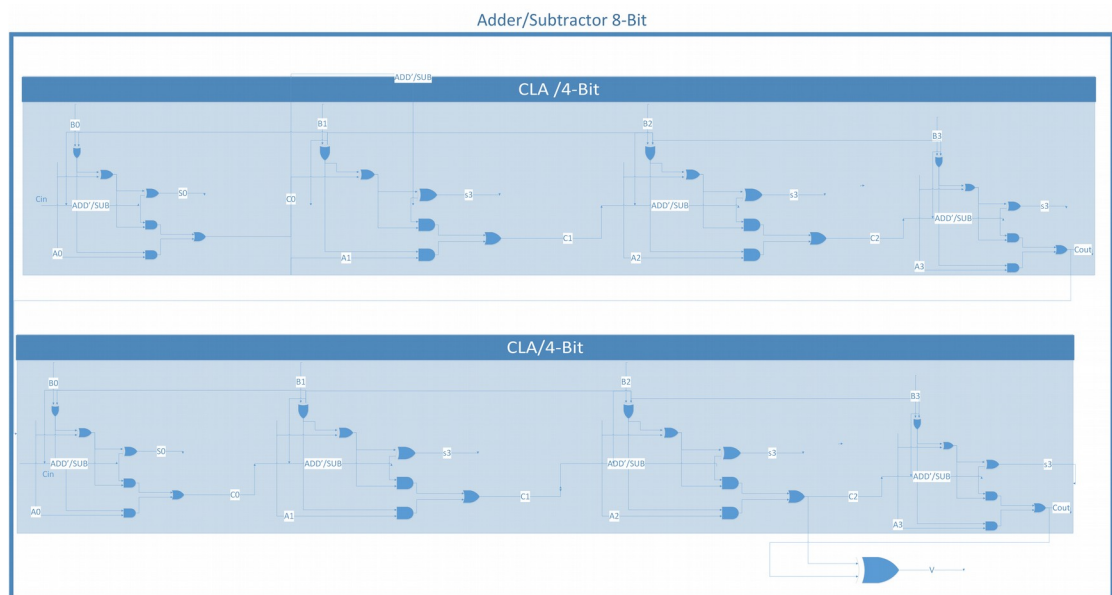

Οι υπόλοιποι μηχανισμοί δεν διαφοροποιούνται

Περιγραφή

Το κύκλωμα εξελίσσεται με την αναπαράσταση του τελευταίου σταδίου του καθώς η αναγνώριση κάθε αριθμητικής πράξης συμβαδίζει και με την περάτωση τής. Κάθε πράξη αφορά στην αναγνώριση της από το σύστημα, την ανταπόκριση του συστήματος στην εκάστοτε διαδικασία βημάτων που απευθύνεται στην μνήμη, την εξαγωγή αριθμών και την προσωρινή αποθήκευση τους σε εργαλεία συνδυαστικής λογικής καθώς και την επεξεργασία τους από την δομή του data path επίσης. Το αποτέλεσμα καθοδηγείται από πολυπλέκτες ώστε να καταλήξει η επιθυμητή τιμή στην μνήμη. Η εντολή για εκχώρηση στη μνήμη δίνεται από την fsm που ασχολείται με τη διαδικασία που υλοποιεί την πράξη ενώ η κάθε τέτοια fsm επικοινωνεί με την fsm που ασχολείται με την εισαγωγή/εξαγωγή τιμών. Κάθε τέτοια fsm έχει ως έξοδο ένα σήμα που εκπροσωπεί την

Η λειτουργικότητα της σχεδίασης εκφράζεται ως εξής:

Push=>Εισαγωγή ενός αριθμού των 8 bit στη στοίβα.

Pop=>Αφαίρεση ενός αριθμού των 8 bit από την στοίβα – όχι αφαίρεση σαν πράξη.

Add=> Αποτελείται από 2 καταχωρήσεις pop από την στοίβα (εκχώρηση στους καταχωρητές) – 1 push με την επεξεργασία από τον προσθαφαιρέτη (αποθηκεύεται πρώτα σε έναν 3ο καταχωρητή.)

Sub=> Αποτελείται από 2 καταχωρήσεις pop από την στοίβα (εκχώρηση στους καταχωρητές) – 1 push στην μνήμη μετά την επεξεργασία από τον προσθαφαιρέτη (αποθηκεύεται πρώτα σε έναν 3ο καταχωρητή)

Unary Sub=> Αποτελείται από 1 καταχώρηση pop (εκχώρηση στον καταχωρητή) – 1 push στην μνήμη μετά την επεξεργασία από τον προσθαφαιρέτη

Swap => Αποτελείται από 2 καταχωρήσεις pop (εκχώρηση στον καταχωρητή) – 2 διαδοχικά push στην μνήμη (πρώτα του 2ου καταχωρητή και ύστερα του 1ου)

Ο προσθαφαιρέτης για την πρόσθεση/αφαίρεση χρησιμοποιεί ως ορίσματα τους δυο αριθμούς που κάνει pop ενώ για το εργαλείο επεξεργασίας Unary Sub χρησιμοποιείται το ίδιο module με την διαφορά ότι το 1ο όρισμα είναι το “00000000” και το 2ο είναι αυτό που γίνεται pop. Σημειώνεται επίσης ότι υπάρχει και μηχανισμός εντοπισμού υπερχειλίσσης(λογικές πύλες) στον προσθαφαιρέτη που αναλογεί σε αναγνώριση της συγκεκριμένης κατάστασης από τα 7-segment display


Παραμένει το κουμπί εναλλαγής mode χωρίς καμιά τροποποίηση – Καθοδηγείται από την fsm ως εξής

Present State	Mode 0	Mode 1	Mode 2
Next State (Εναλλαγή Mode)	Mode 1	Mode 2	Mode 0

Στα διάφορα mode παραμένουν οι αντίστοιχες πράξεις (όπως στα προηγούμενα εργαστήρια)


Το Reset παραμένει στο κουμπί και η λειτουργία του δεν διαφοροποιείται αφού προκαλεί την αρχικοποίηση της μνήμης ,αντιγράφονται δηλαδή οι εκχωρημένες τιμές σε κάθε νέα εγγραφή. Στην αδράνεια είναι η μόνη λειτουργία που μπορεί να πραγματοποιηθεί. Φυλάσσονται τα χαρακτηριστικά των μετρητών της στοίβας ως έχουν όπως και τα υπόλοιπα γνωρίσματα της μνήμης (comparators, muxes, stack)

 Μόνη τροποποίηση στην οποία έχει επιδεχθεί το σύστημα του display αφορά την αριθμητική υπερχείλιση . Το κύκλωμα αδρανοποιείται και στο αριθμητικό overflow αποτυπώνοντας ανάλογο σήμα overflow (Στο αριθμητικό overflow δείχνουμε την απεικόνιση OF χρησιμοποιώντας τα δυο αριστερότερα segment




Κυματομορφές-Προσομοίωση

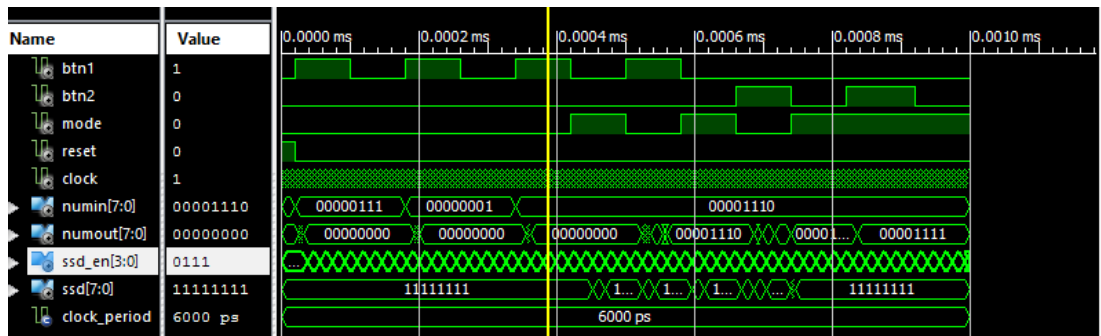
Παρουσιάζουμε τις κυματομορφές του συστήματος.



 Στην παραπάνω κυματομορφή ελέγχουμε τις πράξεις πρόσθεσης και μοναδιαίας αφαίρεσης. Αρχικά εισάγουμε τιμές στην μνήμη για να είναι αποτελεσματικές οι πράξεις (βλέπουμε ότι στο numout υπάρχει ένας θόρυβος της κυματομορφής γιατί εκχωρείται η τιμή



Η μηχανή που εκπροσωπεί το mode 1 στέλνει σήμα ενεργοποίησης της μηχανής που αφορά την πρόσθεση ώστε να ξεκινήσει η διαδικασία, δηλαδή να πραγματοποιηθούν αποβολές τιμών από την μνήμη – πρώτα της κορυφής και ύστερα της προηγούμενης τιμής . Την ευθύνη της εκτέλεσης αποβολής τιμών από την μνήμη την διαχειρίζεται η μηχανή που αφορά το Mode 0 – είναι η μόνη που εκτελεί push/pop η οποία ενεργοποιείται από την fsm κάθε πράξης .

 


Name	Value	
a_signal	1	
as_pushen	0	
as_popen	0	
addsubaction	0	
addorsubsigna	1	
fsm0en	1	
reg0act	1	
reg2act	0	
reg1act	0	
currents	dn1	dn0 < outelem > writer0 < outelem > writer1 < waits > writest
nexts	dn1	< outelem > writer0 < outelem > writer1 < waits > writest dn1
push	0	
pop	0	
modeen	1	
u_d	1	
counteren	0	
stackwrite	1	
currents	push1s	dn < pops > dn < pops > dn < push1s > push2s
nexts	push2s	dn < pops > dn < pops > dn < push1s > push2s
a[4:0]	00001	00011 < > 00010 < > 00001
d[7:0]	00001111	UUUUUUUU 00001111
clk	0	
we	1	
spo[7:0]	00000001	00000000 < > 00001110 < > 00000001 < > 00001111


- Τοποθέτηση τιμής
- Αύξηση μετρητή

Τα αποτελέσματα των πράξεων περνάνε από έναν πολυπλέκτη 4-1 όπου το αποτέλεσμα της πρόσθεσης και της αφαίρεσης είναι βραχυκυκλωμένο ενώ το σήμα έλεγχου είναι ένας κωδικοποιητής που έχει ως σήματα εισόδου το σήμα που δηλώνει την πράξη που διαλέγεται

Η προσομοίωση συνεχίζεται επιτελώντας την πράξη Unary . Ομοίως υπάρχει η μηχανή του mode 2 που στέλνει σήμα στην μηχανή που αφορά την μοναδιαία αφαίρεση και εκείνη ενεργοποιεί την μηχανή push/pop . Υπενθυμίζεται ότι απαιτείται ένας κύκλος ρολογιού κάθε φορά που μια μηχανή πρέπει να στείλει μήνυμα ενεργοποίησης στην άλλη – χρειάζεται επίσης ένας κύκλος αφού ενεργοποιηθεί η μηχανή να ξεκινήσει την διαδικασία).

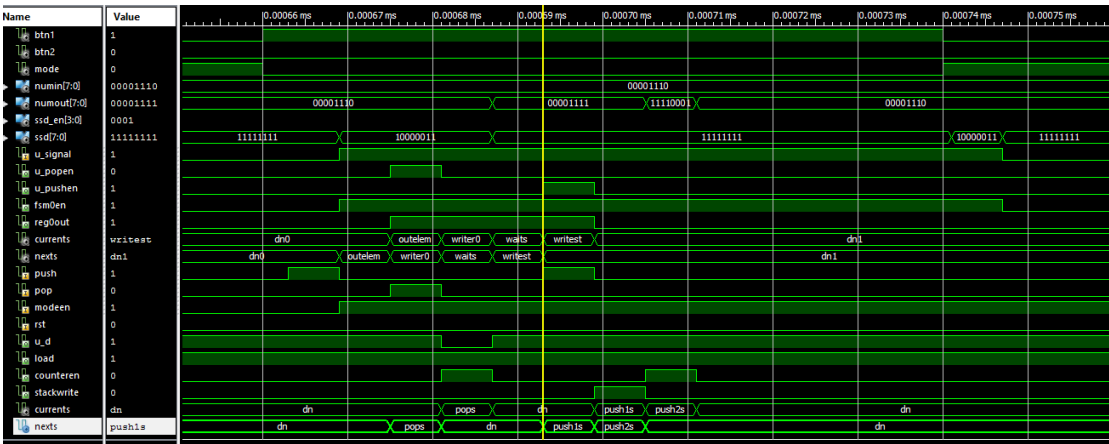


Για ModeEn=1 θέλουμε να περάσουμε την τιμή που βρίσκεται στην κορυφή της στοίβας (το αποτέλεσμα της πρόσθεσης) σε καταχωρητή. Δίνεται η εντολή pop . Η μηχανή της πράξης επικοινωνεί με την Push/pop μηχανή και η τιμή σώζεται στον καταχωρητή . Η μοναδιαία αφαίρεση υλοποιείται από έναν προσθαφαιρέτη που διαθέτει στον πρώτο τελεστέο τον αριθμό “00000000” και ο δεύτερος τελεστέος εισέρχεται μέσα από πύλες XOR.

 


Τελεστές	Πρόσθεση	Μοναδιαία αφαίρεση
00001110	00001111	11110001
00000001		

 
Θέλοντας να επαληθεύσουμε την αλληλουχία των πράξεων εκτελούμε μια αποβολή τιμής



 Συνεχίζεται η ανάλυση του συστήματος διερευνώντας στην προσομοίωση την τελευταία πράξη της εναλλαγής τιμών



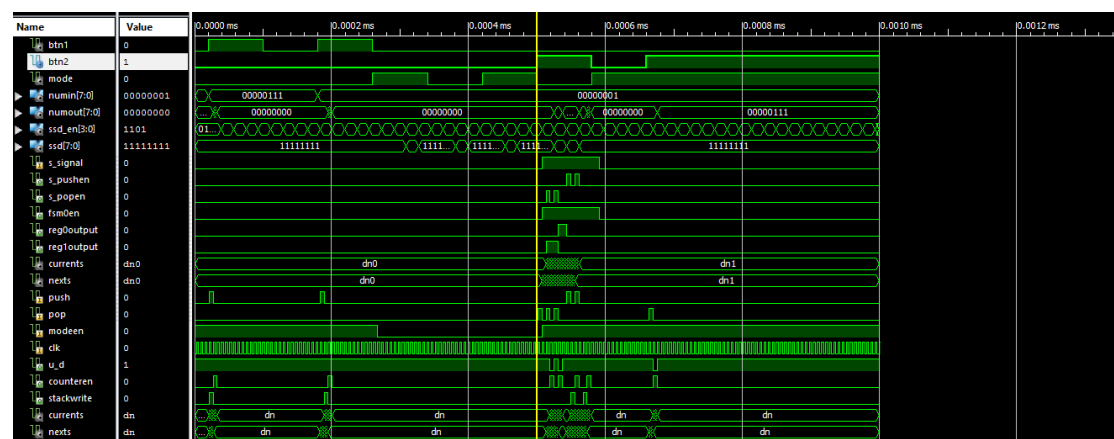
Με την ίδια μεθοδολογία ανακαλύπτουμε τις πτυχές που αναπτύσσει και η πράξη swar. Η fsm του mode 2 όταν βρίσκεται σε σύνδεση λειτουργίας και επιλεχθεί η εκπλήρωση του swar, τότε δίνεται σήμα ενεργοποίησης στην μηχανή που ανάγεται στη διεργασία της πράξης και αυτή με της σειρά της επικοινωνεί με την μηχανή push/pop.



Για την ανταλλαγή τιμών απαιτούνται 2 δράσεις pop (πρώτα της κορυφής και της προηγούμενη τιμής αυτής) και στη συνέχεια 2 δράσεις push (πρώτα της κορυφής και της τιμής κάτω της κορυφής). Μελετώντας την μηχανή για το Push/pop παρατηρούμε ότι δέχεται το σήμα pop από την μηχανή για το swar, η μηχανή έχει από εδώ και πέρα ανοιχτό enable και ξεκινάει το pop όπου το enable που βγαίνει στον counter ενεργοποιείται ενώ το up/down γίνεται 0 και ο μετρητής μετράει προς τα κάτω. Επαναλαμβάνεται και για το 2ο pop. Οι τιμές αποθηκεύονται στους 2ο καταχωρητές. Η διαδικασία εξακολουθεί να διεξάγεται εκτελώντας τα push. Δίνονται τα push από την μια μηχανή στην άλλη και γράφονται οι τιμές (το stack write γίνεται 1 και στο επόμενο state αυξάνεται ο counter)

Οι καταχωρητές οδηγούνται από έναν πολυπλέκτη 2 σε 1 του οποίου η έξοδος βρίσκεται ως είσοδο στον πολυπλέκτη 4-1 ώστε μια φορά να περνάει η τιμή του ενός και μία του άλλου καταχωρητή ώστε να διοχετεύονται με επάρκεια στην μνήμη.

 Ελέγχουμε την αλλαγή των τιμών κάνοντας Pop μια τιμή




Μνήμη πριν το Swar (σειρά από κάτω προς τα πάνω)	Μνήμη μετά το Swar (σειρά από κάτω προς τα πάνω)	Μνήμη μετά το Pop (σειρά από κάτω προς τα πάνω)
00000001	00000111	
00000111	00000001	00000001

Η έξοδος του πολυπλέκτη 4-1 πηγαίνει σε ένα πολυπλέκτη 2-1 που έχει ως δεύτερη είσοδο τον αριθμό προς εισαγωγή ενώ ως σήμα ελέγχου δέχεται μια πύλη OR 3 εισόδων που έχει τα enable εξόδου που ενεργοποιούν την μηχανή Push/pop. Δηλαδή εφόσον πατήθηκε κάποια διεργασία mode εκτός του 0 τότε το αποτέλεσμα προέρχεται από τον

πολυπλέκτη 4-1 Αλλιώς γίνεται εισαγωγή κάποιου αριθμού.

Σε μια τελευταία προσομοίωση για να ελέγξουμε την ακινητοποίηση του συστήματος στο αριθμητικό overflow πραγματοποιούμε εισαγωγή 2 αριθμών ικανών να παρασκευάσουν υπερχειλίση και τους προσθέτουμε

Ιδού τα αποτελέσματα

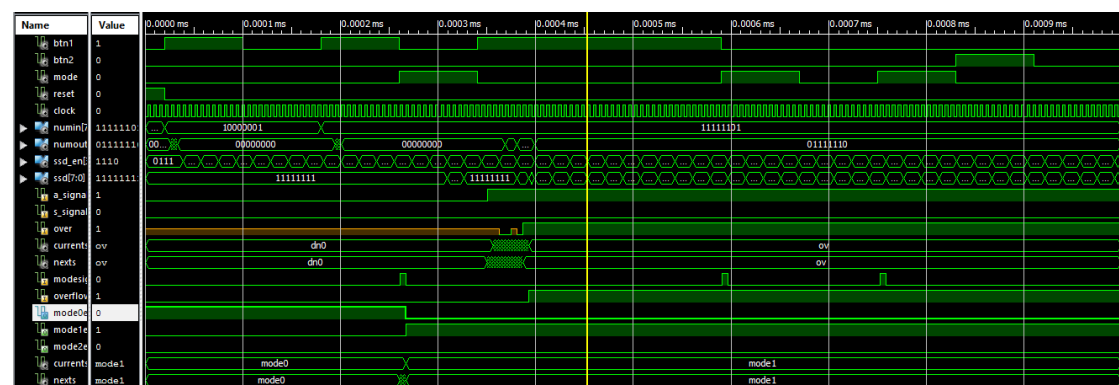

(Στην προσομοίωση έχουμε προσθέσει και την μηχανή που αλλάζει Modes αλλά και την μηχανή της πράξης add)

Διακρίνουμε τα εξής :

- Προσθέτουμε 2 αριθμούς $10000001 + 11110001 = 01111110$
- Η αρμόδια fsm για τα modes παραμένει στο mode ενώ περιμένει reset για να αρχικοποιηθεί

- | Name | Value | 0.00036 ms | 0.00038 ms | 0.00040 ms | 0.00042 ms | 0.00044 ms | 0.00046 ms | 0.00048 ms | 0.00050 ms | 0.00052 ms | 0.00054 ms |
|-----------|----------|------------|------------|------------|------------|------------|------------|------------|------------|------------|------------|
| btn1 | 1 | | | | | | | | | | |
| btn2 | 0 | | | | | | | | | | |
| mode | 0 | | | | | | | | | | |
| reset | 0 | | | | | | | | | | |
| clock | | | | | | | | | | | |
| numin[7] | 11111110 | | | | | | 11111101 | | | | |
| numout | 01111110 | 00000000 | 11111101 | 10000001 | | | | 01111110 | | | |
| ssd_en[7] | 1110 | 1101 | 1110 | 0111 | 1011 | 1101 | 1110 | 0111 | 1011 | 1101 | 1110 |
| ssd[7:0] | 11111111 | 11111111 | 00010001 | 00 | 10000011 | 01110001 | 11111111 | 00000011 | 10000011 | 01110001 | 11111111 |
| a_signal | 1 | | | | | | | | | | |
| over | 0 | | | | | | | | | | |
| currents | ov | dn | out... | wn... | waitb | wn... | | | | | |
| nexts | ov | | | | | | ov | | | | |
| modesh | 0 | | | | | | ov | | | | |
| overflow | 1 | | | | | | | | | | |
| mode0e | 1 | | | | | | | | | | |
| mode1e | 1 | | | | | | | | | | |
| mode2e | 0 | | | | | | | | | | |
| currents | mode1 | | | | | | mode1 | | | | |
| nexts | mode1 | | | | | | mode1 | | | | |

Υστερα από το πέρας της εργαστηριακής άσκησης δημιουργούνται αξιόλογα συμπεράσματα πάνω στην μελέτη και σχεδίαση υλικού . Αδιαμφισβήτητα η σχεδίαση και η επεξεργασία δεδομένων ενός προβλήματος αντιμετωπίζεται πλέον με μεγαλύτερη ευχέρεια όσον αφορά τον προγραμματισμό καθώς η χρησιμοποίηση των κατάλληλων εργαλείων σχεδίασης (μηχανές fsm, πολυπλέκτες , κωδικοποιητές και λοιπά συνδυαστικά και ακολουθιακά κυκλώματα) προσδίδει εμπειρία και ευρύτερη γνώση της δουλειάς για κάθε μηχανισμό. Η συνολική σχεδίαση διαθέτει ενδιαφέροντες λειτουργικότητες (σχεδιασμός μηχανής που εκτελεί συγκεκριμένες αριθμητικές και μη λειτουργίες , 7s displays , αρχικοποίηση , εναλλαγές καταστάσεων) που εκφράζονται σε πραγματικές δράσεις πάνω στην αναδιατασσόμενη συσκευή και παρουσιάζουν μεγάλο φάσμα των δυνατοτήτων του υλικού . Η υλοποίηση της δομής της αριθμομηχανής ολοκληρώθηκε.

- Στον κώδικα δεν περιλαμβάνονται οι FSM (ssdFsm) για τα Seven segment display και την στοίβα (FSM0,FSM1,FSM2, ModeController , ASFsm, Ufsm, SwapFSM) καθώς επίσης και τα singe pulse generator.

TOP

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

USE IEEE.STD_LOGIC_ARITH.ALL;
```

entity Top is

Port (BTN1 : in STD_LOGIC;

BTN2 : in STD_LOGIC;

Mode: in STD_LOGIC;

Reset : in STD_LOGIC;

Clock : in STD_LOGIC;

NUMIN : in STD_LOGIC_VECTOR (7 downto 0);

NUMOUT : out STD_LOGIC_VECTOR (7 downto 0);

SSD_EN : out STD_LOGIC_VECTOR (3 downto 0);

SSD : out STD_LOGIC_VECTOR (7 downto 0));

end Top;

architecture Behavioral of Top is

signal StackPointer:std_logic_vector(4 downto 0):="00000";

SIGNAL BTN1P, BTN2P, UDP, LD_P, WriteEnable,FlagEnable, SecCounEn, OVFP, CounterEnable,
FullSignal, EmptySignal : STD_LOGIC;

SIGNAL out_tos,out_tosm1: STD_LOGIC_VECTOR(4 DOWNT0 0);

signal StackOut:STD_LOGIC_VECTOR(7 DOWNT0 0):="00000000";

```

signal Mode0Sig,Mode1Sig,Mode2Sig,ModePipe:std_logic:='0';

    signal AddOut,SubOut:std_logic:='0';

    signal UnarySubOut,SwapOut:std_logic:='0';

signal Reg0Val,Reg1Val,Reg2Val:std_logic_vector(7 downto 0);

    signal RegEn0,RegEn1,RegEn2:std_logic:='0';

    signal actionSignal:std_logic;

signal UnaryVal:std_logic_vector(7 downto 0);

    signal boxCarry,boxV:std_logic:='0';

SIGNAL boxResult:STD_LOGIC_VECTOR(7 DOWNT0 0);

    signal PopSignal,PushSignal:std_logic;

    signal PopSign,PushSign:std_logic;

    signal PopS,PushS:std_logic;

    signal R0En,R1En:std_logic;

    signal enableReg0,enableReg1:std_logic;

signal temp1,temp2,temp3,temp4,temp5,temp6,temp7,temp9,temp10:std_logic:='0';

SIGNAL multi2v1_1Val,multi2v1_2Val,multi4v1Val:std_logic_vector(7 downto
0):="00000000";

signal FSM0En1,FSM0En2,FSM0En3:std_Logic;

    signal addsubsig:std_Logic;

    signal overflowSignal:std_logic;

signal signCoder:std_logic_vector(1 downto 0);

```

COMPONENT singlepulsegen IS

```

Port ( clk          : in std_logic;          -- connect it to the Clock of the board

      rst           : in std_logic;          -- connect it to the Reset Button of the
                                         board

      input         : in std_logic;          -- connect it to the Push Button of the board

```

```
output    : out std_logic      -- connect it to the input of your circuit
    );
```

```
end COMPONENT;
```

```
component Reg is
```

```
Port ( Clock : in  STD_LOGIC;
```

```
D : in  STD_LOGIC_VECTOR(7 DOWNTO 0);
```

```
Enable : in  STD_LOGIC;
```

```
Q : out  STD_LOGIC_vector(7 downto 0));
```

```
end component;
```

```
COMPONENT FSM0 IS
```

```
Port ( Push : in  STD_LOGIC;
```

```
Pop : in  STD_LOGIC;
```

```
Clk : in  STD_LOGIC;
```

```
ModeEn:in std_logic;
```

```
arOv:in std_logic;
```

```
Rst : in  STD_LOGIC;
```

```
Empty : in STD_LOGIC;
```

```
Full: in STD_Logic;
```

```
U_D : out STD_LOGIC;
```

```
LOAD : out STD_LOGIC;
```

```
CounterEn : out STD_LOGIC;
```

```
StackWrite : out STD_LOGIC;
```

```
STACK_OVF : out STD_LOGIC);
```

```
END COMPONENT;
```

component FSM1 is

Port(Clk:in std_logic;

Rst:in std_logic;

ModeEn:in std_logic;

Add:in std_logic;

Sub:in std_logic;

AddOutput:out std_logic;

SubOutput:out std_logic);

end component;

component FSM2 is

Port(Clk:in std_logic;

Rst:in std_logic;

ModeEn:in std_logic;

UnarySub:in std_logic;

Swap:in std_logic;

UnarySubOutput:out std_logic;

SwapOutput:out std_logic);

end component;

COMPONENT Comparator_Equality is

Port (B1 : in STD_LOGIC_VECTOR (4 downto 0);

B2 : in STD_LOGIC_VECTOR (4 downto 0);

Y1 : out STD_LOGIC);

end COMPONENT;

COMPONENT STACK IS

```
PORT ( a: in STD_LOGIC_VECTOR(4 downto 0);  
      d: in STD_LOGIC_VECTOR(7 downto 0);  
      clk: in STD_LOGIC;  
      we: in STD_LOGIC;  
      spo: out STD_LOGIC_VECTOR(7 downto 0));  
END COMPONENT;
```

COMPONENT COUNTER IS

```
Port ( En : in STD_LOGIC;  
input : in STD_LOGIC_Vector(4 downto 0);  
output : out STD_LOGIC_Vector(4 downto 0);  
      Clock : in STD_LOGIC;  
      Load : in STD_LOGIC;  
      U_D : in STD_LOGIC);  
end COMPONENT;
```

COMPONENT SSDController is

```
PORT (Clk : in STD_LOGIC;  
      Rst : in STD_LOGIC;  
      Empty : in STD_LOGIC;  
      Full : in STD_LOGIC;  
      Stack_OVF : in STD_LOGIC;  
      overflowAr:in std_logic;  
      A:in std_logic;
```

```

        S:in std_logic;

        U:in std_logic;

        SWAP:in std_logic;

        Mode0:in std_logic;

        Mode1:in std_logic;

        Mode2:in std_logic;

        ANcontrol : out STD_LOGIC_VECTOR(3 downto 0);

        SSControl : out STD_LOGIC_VECTOR(7 downto 0));

    end COMPONENT;

```

Component ModeFsm is

```

Port ( Clock : in  STD_LOGIC;

        Reset : in  STD_LOGIC;

        ModeSignal : in  STD_LOGIC;

        overflow:in std_logic;

        Mode0En : out  STD_LOGIC;

        Mode1En : out  STD_LOGIC;

        Mode2En : out  STD_LOGIC);

    end component;

```

component UnaryOp is

```

Port ( NIn : in  STD_LOGIC_vector(7 downto 0);

        NOut : out  STD_LOGIC_vector(7 downto 0));

    end component;

```

COMPONENT ASFsm is

```

Port ( Clk : in STD_LOGIC;

      Rst : in STD_LOGIC;

      A_Signal : in STD_LOGIC;

      OVER:in std_logic;

      S_Signal : in STD_LOGIC;

      AS_PushEn : out STD_LOGIC;

      AS_PopEn : out STD_LOGIC;

      AddSubAction:out std_logic;

      AddOrSubSignal:out std_logic;

      FSM0En:out std_logic;

      Reg2Act:out std_logic;

      overflow:out std_logic;

      Reg0Act : out STD_LOGIC;

      Reg1Act : out STD_LOGIC);

end COMPONENT;

```

component CLA8BIT is

```

Port ( A : in STD_LOGIC_VECTOR (7 downto 0);

      B : in STD_LOGIC_VECTOR (7 downto 0);

      M : in STD_LOGIC;

      Result : out STD_LOGIC_VECTOR (7 downto 0);

      COUT : out STD_LOGIC;

      V : out STD_LOGIC);

end component;

```

component UFsm is

Port (Clock : in STD_LOGIC;

Reset : in STD_LOGIC;

U_Signal : in STD_LOGIC;

U_PopEn : out STD_LOGIC;

U_PushEn : out STD_LOGIC;

FSM0En:out std_logic;

Reg0Out: out STD_LOGIC);

end component;

component SwapFSM is

Port (Clk : in STD_LOGIC;

Rst : in STD_LOGIC;

S_Signal : in STD_LOGIC;

S_PushEn : out STD_LOGIC;

FSM0En:out std_logic;

S_PopEn : out STD_LOGIC;

Reg0Output : out STD_LOGIC;

Reg1Output : out STD_LOGIC);

end component;

COMPONENT Multiplexer2v1 is

Port (Q0 : in STD_LOGIC_VECTOR (7 downto 0);

Q1 : in STD_LOGIC_VECTOR (7 downto 0);

Sign : in STD_LOGIC;

OUTM : out STD_LOGIC_VECTOR (7 downto 0));

```
end COMPONENT;
```

```
component Multiplexer4v1 is
```

```
Port ( Q0 : in STD_LOGIC_VECTOR (7 downto 0);
```

```
      Q1 : in STD_LOGIC_VECTOR (7 downto 0);
```

```
      Q2 : in STD_LOGIC_VECTOR (7 downto 0);
```

```
      Q3 : in STD_LOGIC_VECTOR (7 downto 0);
```

```
      Sign : in STD_LOGIC_VECTOR (1 downto 0);
```

```
      OUTM : out STD_LOGIC_VECTOR (7 downto 0));
```

```
end component;
```

```
component Coder is
```

```
Port ( Input : in STD_LOGIC_VECTOR (3 downto 0);
```

```
      Output : out STD_LOGIC_VECTOR (1 downto 0));
```

```
end component;
```

```
begin
```

```
    coderSign:Coder
```

```
port map(Input(0)=>NOT AddOut,
```

```
         Input(1)=>NOT SubOut,
```

```
         Input(2)=>NOT UnarySubOut,
```

```
         Input(3)=>NOT SwapOut,
```

```
         Output=>signCoder);
```

SFsm:SwapFSM

```
Port map(Clk=>Clock,  
         Rst=>Reset,  
         S_Signal=>SwapOut,  
         S_PopEn=>PopS,  
         FSM0En=>FSM0En3,  
         S_PushEn=>PushS,  
         Reg0Output=>enableReg0,  
         Reg1Output=>enableReg1);
```

Multi4v1:Multiplexer4v1

```
port map(Q0=>Reg2Val,  
         Q1=>Reg2Val,  
         Q2=>UnaryVal,  
         Q3=>multi2v1_1Val,  
         Sign=>signCoder,  
         OUTM=>multi4v1Val);
```

UnFsm:UFsm

```
Port map(Clock=>Clock,  
         Reset=>Reset,  
         U_Signal=>UnarySubOut,  
         U_PopEn=>PopSign,  
         U_PushEn=>PushSign,
```

```

        FSM0En=>FSM0En2,

        Reg0Out=>R0En);

temp9<=FSM0En1 or FSM0En3 or FSM0En2;

StackMultiplexer:Multiplexer2v1

    port map(Q0=>NUMIN,

        Q1=>multi4v1Val,

        Sign=>temp9,

        OUTM=>multi2v1_2Val);

swapMultiplexer:Multiplexer2v1

    port map(Q0=>Reg0Val,

        Q1=>Reg1Val,

        Sign=>enableReg1,

        OUTM=>multi2v1_1Val);

UnaryACT: UnaryOp

    PORT MAP(NIn=>Reg0Val,

        NOut=>UnaryVal);

temp4<=RegEn0 or R0En or enableReg0;

Reg0: Reg

    PORT MAP(Clock => Clock,

        D => StackOut,

```

Enable =>temp4,

Q => Reg0Val);

temp5<= RegEn1 or R1En or enableReg1;

Reg1: Reg

PORT MAP(Clock => Clock,

D => StackOut,

Enable =>temp5,

Q => Reg1Val);

Reg2: Reg

Port map(CLOCK=>Clock,

D=>boxResult ,

Enable=>RegEn2,

Q=>Reg2Val);

AddSubFSM: ASFsm

PORT MAP(Clk=>Clock,

Rst=>Reset,

A_Signal=>AddOut,

S_Signal=>SubOut,

OVER=>boxV,


```

AS_PushEn=>PushSignal,
AS_PopEn=>PopSignal,
FSM0En=>FSM0En1,
AddSubAction=>actionSignal,
AddOrSubSignal=>addsubsig,
Reg0Act=>RegEn0,
overflow=>overflowSignal,
Reg2Act=>RegEn2,
Reg1Act=>RegEn1);

```

AddSubBox: CLA8BIT

```

PORT MAP(A=>Reg0Val,
         B=>Reg1Val,
         M=>actionSignal,
         Result=>boxResult,
         COUT=>boxCarry,
         V=>boxV);

```

SPG0 : singlepulsegen

```

PORT MAP( clk => Clock,
         rst => Reset,
         input => BTN1,
         output => BTN1P);

```

SPG1 : singlepulsegen

```
PORT MAP( clk => Clock,  
          rst => Reset,  
          input => BTN2,  
          output => BTN2P);
```

SPG2 : singlepulsegen

```
Port Map(clk=>Clock,  
          rst=>Reset,  
          input=>Mode,  
          output=>ModePipe);
```

```
temp1<=      BTN1P or (PushSignal or PushSign or PushS) ;  
temp2<=      BTN2P or (PopSignal or PopSign or PopS);  
temp3<=      Mode0Sig OR FSM0En1 or FSM0En2 or FSM0En3;  
FSM_M0 : FSM0  
PORT MAP( Push => temp1,  
          Pop => temp2,  
          Clk => Clock,  
          ModeEn=>temp3,  
          Rst => Reset,  
          U_D => UDP,  
          Empty => EmptySignal,  
          arOv=>overflowSignal,
```

```

Full => FullSignal,

LOAD => LD_P,

CounterEn => CounterEnable,

StackWrite => WriteEnable,

STACK_OVF =>OVFP);

```

FSM_M1:FSM1

```

Port MAP(Clk=>Clock,

Rst=>Reset,

ModeEn=>Mode1Sig,

Add=>BTN1P ,

Sub=>BTN2P ,

AddOutput=>AddOut,

SubOutput=>SubOut);

```

FSM_M2:FSM2

```

Port MAP(Clk=>Clock,

Rst=>Reset,

ModeEn=>Mode2Sig,

UnarySub=>BTN1P AND (NOT overflowSignal),

Swap=>BTN2P AND (NOT overflowSignal),

UnarySubOutput=>UnarySubOut,

SwapOutput=>SwapOut);

```

```

temp10<=overflowSignal or OVFP;

```

ModeController:ModeFsm

```
Port map(Clock=>Clock,  
         Reset=>Reset,  
         ModeSignal=>ModePipe,  
         overflow=>temp10,  
         Mode0En=>Mode0Sig,  
         Mode1En=>Mode1Sig,  
         Mode2En=>Mode2Sig);
```

myStack : STACK

```
PORT MAP( a => out_tos, --<<  
         d => multi2v1_2Val,  
         clk => Clock,  
         we => WriteEnable,  
         spo => StackOut);
```

Counter2 : COUNTER

```
PORT MAP( input => StackPointer,  
         U_D => UDP,  
         En => CounterEnable,  
         Clock => Clock,  
         Load=>LD_P,  
         output => out_tos);
```

Counter1 : COUNTER

```
PORT MAP( input => StackPointer,  
          U_D => UDP,  
          En => SecCounEn, --Blepe telos kodika  
          Clock => Clock,  
          Load=>LD_P,  
          output => out_tosm1);
```

EmptyComparator : Comparator_Equality

```
PORT MAP (B1 => "00000",  
          B2 => out_tos,  
          Y1 => EmptySignal);
```

FullComparator : Comparator_Equality

```
PORT MAP (B1 => "11111",  
          B2 => out_tos,  
          Y1 => FullSignal);
```

ssdControl: SSDController

```
PORT MAP(Clk => Clock,  
          Rst => Reset,  
          Empty => EmptySignal,  
          Full => FullSignal,  
          A=>AddOut,  
          S=>SubOut,
```

```

        U=>UnarySubOut,

        SWAP=>SwapOut,

        Mode0=>Mode0Sig,

        Mode1=>Mode1Sig,

        Mode2=>Mode2Sig,

        Stack_OVF=> OVFP,

        overflowAr=>overflowSignal,

        ANControl => SSD_EN,

        SSControl => SSD);

secondCounterEnable :PROCESS(EmptySignal,UDP,out_tos)

    BEGIN

    IF ((EmptySignal = '1')or (UDP='0' AND out_tos="00001")) THEN --<<<<<

        FlagEnable <= '0';

        ELSE

        FlagEnable <= '1';

        END IF;

    END PROCESS;

    NUMOUT<=StackOut;

    SecCounEn <= CounterEnable AND FlagEnable;

end behavioral;

```

CODER

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;


entity Coder is
Port ( Input : in  STD_LOGIC_VECTOR (3 downto 0);
      Output : out STD_LOGIC_VECTOR (1 downto 0));
end Coder;


architecture Behavioral of Coder is

begin

    coder : process(Input)

    begin

        IF(Input = "1110") THEN Output <= "00";
        ELSIF(Input = "1101") THEN Output <= "01";
        ELSIF(Input = "1011") THEN Output <= "10";
        ELSIF(Input = "0111") THEN Output <= "11";

        ELSE Output <= "00";

        END IF;

    end process;

end Behavioral;
```

MULTIPLEXER 4-1

-- any Xilinx primitives in this code.

--library UNISIM;

--use UNISIM.VComponents.all;

entity Multiplexer4v1 is

Port (Q0 : in STD_LOGIC_VECTOR (7 downto 0);

Q1 : in STD_LOGIC_VECTOR (7 downto 0);

Q2 : in STD_LOGIC_VECTOR (7 downto 0);

Q3 : in STD_LOGIC_VECTOR (7 downto 0);

Sign : in STD_LOGIC_VECTOR (1 downto 0);

OUTM : out STD_LOGIC_VECTOR (7 downto 0));

end Multiplexer4v1;

architecture Behavioral of Multiplexer4v1 is

begin

process(Sign,Q0,Q1,Q2,Q3)

BEGIN

if(Sign="00") then

OUTM<=Q0;

ELSIF Sign<="01" then


```

        OUTM<=Q1;
    ELSIF Sign<="10" then
        OUTM<=Q2;
    ELSIF Sign<="11" then
        OUTM<=Q3;
    ELSE OUTM<=Q0;
    END IF;
END PROCESS;
end Behavioral;

```

MULTIPLEXER 2-1

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Multiplexer2v1 is
    Port ( Q0 : in  STD_LOGIC_VECTOR (7 downto 0);
          Q1 : in  STD_LOGIC_VECTOR (7 downto 0);
          Sign : in  STD_LOGIC;
          OUTM : out STD_LOGIC_VECTOR (7 downto 0));
end Multiplexer2v1;

```

architecture Behavioral of Multiplexer2v1 is

```
begin
process(Q0,Q1,Sign)
begin
if Sign='0' then
OUTM<=Q0;
ELSIF Sign='1' then
OUTM<=Q1;
ELSE
OUTM<="00000000";
END IF;
END PROCESS;

end Behavioral;
```

UNARY SUBTRACTOR

```
-----
-----

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;
```

entity UnaryOp is

```
Port ( NIn : in STD_LOGIC_vector(7 downto 0);
```

```
NOut : out STD_LOGIC_vector(7 downto 0));
```

```
end UnaryOp;
```

architecture Behavioral of UnaryOp is

COMPONENT CLA8BIT is

```
Port ( A : in STD_LOGIC_VECTOR (7 downto 0);
```

B : in STD_LOGIC_VECTOR (7 downto 0)

M : in STD LOGIC

Result : out STD LOGIC VECTOR (7 downto 0)

COUT : out STD_LOGIC

V : out STD_LOGIC)

end component

begin

```
complement2s : CLA8BIT PORT MAP(A=>"00000000")
```

$$B \Rightarrow N \ln,$$

M=>'1',

```
Result=>NOut);
```

end Behavioral

REGISTER

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;


entity Reg is
    Port ( Clock : in  STD_LOGIC;
          D : in  STD_LOGIC_VECTOR(7 DOWNT0 0):="00000000";
          Enable : in  STD_LOGIC;
          Q : out STD_LOGIC_vector(7 downto 0));
end Reg;


architecture Behavioral of Reg is

    begin

        process(Clock,Enable)

            begin

                If rising_edge(Clock) then

                    if Enable='1' then

                        Q<=D;

                    end if;

                end if;

            end process;

end process;
```

end Behavioral;

ADDER-SUBTRACTOR

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity CLA8BIT is

Port (A : in STD_LOGIC_VECTOR (7 downto 0);

B : in STD_LOGIC_VECTOR (7 downto 0);

M : in STD_LOGIC;

Result : out STD_LOGIC_VECTOR (7 downto 0);

COUT : out STD_LOGIC;

V : out STD_LOGIC);

end CLA8BIT;

architecture Behavioral of CLA8BIT is

component CLA is

Port (A : in STD_LOGIC_VECTOR (3 downto 0);

B : in STD_LOGIC_VECTOR (3 downto 0);

M : in STD_LOGIC;

Cin : in STD_LOGIC;

SUM : out STD_LOGIC_VECTOR (3 downto 0);

V:out std_logic;

Cout: out STD_LOGIC

);

end component;

```

        signal Csignal:std_logic;

        begin

    CLA1: CLA PORT MAP (A(0)=>A(0),

                                A(1)=>A(1),

                                A(2)=>A(2),

                                A(3)=>A(3),

                                B(0)=>B(0),

                                B(1)=>B(1),

                                B(2)=>B(2),

                                B(3)=>B(3),

                                M=>M,

                                Cin=>M,

                                SUM(0)=>Result(0),

                                SUM(1)=>Result(1),

                                SUM(2)=>Result(2),

                                SUM(3)=>Result(3),

                                Cout=>Csignal

                                );

    CLA2: CLA PORT MAP (A(0)=>A(4),

                                A(1)=>A(5),

                                A(2)=>A(6),

                                A(3)=>A(7),

                                B(0)=>B(4),

                                B(1)=>B(5),

                                B(2)=>B(6),

```

```
B(3)=>B(7),  
  
M=>M,  
  
Cin=>Csignal,  
  
SUM(0)=>Result(4),  
  
SUM(1)=>Result(5),  
  
SUM(2)=>Result(6),  
  
SUM(3)=>Result(7),  
  
Cout=>COUT,  
  
V=>V);
```

```
end Behavioral;
```

COUNTER

```
library IEEE;  
  
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity COUNTER is
```

```
Port ( En : in  STD_LOGIC;  
  
input : in  STD_LOGIC_Vector(4 downto 0);  
  
output : out STD_LOGIC_Vector(4 downto 0);  
  
Clock : in  STD_LOGIC;  
  
Load : in  STD_LOGIC;  
  
U_D : in  STD_LOGIC);
```

```
end COUNTER;
```

```
architecture Behavioral of COUNTER is
```

```
    component MUX4v1 is
```

```
    Port ( Q0 : in  STD_LOGIC;
```

```
          Q1 : in  STD_LOGIC;
```

```
          Q2 : in  STD_LOGIC;
```

```
          Q3 : in  STD_LOGIC;
```

```
          Sign0 : in  STD_LOGIC;
```

```
          Sign1 : in  STD_LOGIC;
```

```
          OUTM : out STD_LOGIC);
```

```
    end component;
```

```
    component FlipFlop is
```

```
    Port ( Clock : in  STD_LOGIC;
```

```
          D : in  STD_LOGIC;
```

```
          Q : out STD_LOGIC);
```

```
    end component;
```

```
    signal mout1,mout2,mout3,mout4,mout5:std_logic;
```

```
    signal fout1,fout2,fout3,fout4,fout5:std_logic;
```

```
    signal ms1,ms2,ms3,ms4,ms5:std_logic;
```

```
    signal nfout1,nfout2,nfout3,nfout4,nfout5:std_logic;
```

```
    signal nload1,nload2,nload3,nload4,nload5:std_logic;
```

```
    signal nUD:std_logic;
```

```
begin
```



```

nUD<=NOT U_D;

ms1<=(En AND U_D) or (En AND nUD);

nfout1<=not fout1;

nload1<=not Load;

M1: MUX4v1 PORT
MAP(Q0=>fout1,Q1=>nfout1,Q2=>input(0),Q3=>input(0),Sign1=>nload1,Sign0=>ms1,OUTM
=>mout1);

F1: FlipFlop PORT MAP(D=>mout1,Clock=>Clock,Q=>fout1);


nload2<=not Load;

nfout2<=not fout2;

ms2<=(En AND fout1 AND U_D) or (En AND nfout1 AND nUD );

M2: MUX4v1 PORT
MAP(Q0=>fout2,Q1=>nfout2,Q2=>input(1),Q3=>input(1),Sign1=>nload2,Sign0=>ms2,OUTM
=>mout2);

F2: FlipFlop PORT MAP(D=>mout2,Clock=>Clock,Q=>fout2);


nload3<=not Load;

nfout3<=not fout3;

ms3<=(En AND fout1 AND fout2 AND U_D) or (En AND nfout1 AND nfout2 AND nUD);

M3: MUX4v1 PORT
MAP(Q0=>fout3,Q1=>nfout3,Q2=>input(2),Q3=>input(2),Sign1=>nload3,Sign0=>ms3,OUTM
=>mout3);

F3: FlipFlop PORT MAP(D=>mout3,Clock=>Clock,Q=>fout3);


nfout4<=not fout4;

nload4<=not Load;

```

```
ms4<=(En AND fout1 AND fout2 AND fout3 AND U_D) or (En AND nfout1 AND nfout2 AND
nfout3 AND nUD);
```

```
M4: MUX4v1 PORT
```

```
MAP(Q0=>fout4,Q1=>nfout4,Q2=>input(3),Q3=>input(3),Sign1=>nload4,Sign0=>ms4,OUTM
=>mout4);
```

```
F4: FlipFlop PORT MAP(D=>mout4,Clock=>Clock,Q=>fout4);
```

```
nload5<=not Load;
```

```
nfout5<=not fout5;
```

```
ms5<=(En AND fout1 AND fout2 AND fout3 AND fout4 AND U_D) or (En AND nfout1 AND
nfout2 AND nfout3 AND nfout4 AND nUD);
```

```
M5: MUX4v1 PORT
```

```
MAP(Q0=>fout5,Q1=>nfout5,Q2=>input(4),Q3=>input(4),Sign1=>nload5,Sign0=>ms5,OUTM
=>mout5);
```

```
F5: FlipFlop PORT MAP(D=>mout5,Clock=>Clock,Q=>fout5);
```

```
output(0)<=fout1;
```

```
output(1)<=fout2;
```

```
output(2)<=fout3;
```

```
output(3)<=fout4;
```

```
output(4)<=fout5;
```

```
end Behavioral;
```

SSDCONTROL

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity SSDController is
```

```
    PORT (Clk : in  STD_LOGIC;
```

```
          Rst : in  STD_LOGIC;
```

```
          Empty : in  STD_LOGIC;
```

```
          Full : in  STD_LOGIC;
```

```
          Stack_OVF : in  STD_LOGIC;
```

```
          overflowAr:in std_logic;
```

```
          A:in std_logic;
```

```
          S:in std_logic;
```

```
          U:in std_logic;
```

```
          SWAP:in std_logic;
```

```
          Mode0:in std_logic;
```

```
          Mode1:in std_logic;
```

```
          Mode2:in std_logic;
```

```
          ANcontrol : out STD_LOGIC_VECTOR(3 downto 0);
```

```
          SSControl : out STD_LOGIC_VECTOR(7 downto 0));
```

```
end SSDController;
```

```
architecture Behavioral of SSDController is
```

```
    Signal CounterPipe : STD_LOGIC;
```

```
    Signal FSMOutPipe : STD_LOGIC_VECTOR(3 downto 0);
```

Signal muxInPipe: STD_LOGIC_VECTOR(31 downto 0);

Signal muxControl : STD_LOGIC_VECTOR(1 downto 0);

COMPONENT BehCounter IS

Port (Clk : in STD_LOGIC;

Rst : in STD_LOGIC;

Q : out STD_LOGIC);

END COMPONENT;

COMPONENT SSDFSM is

Port (Clk : in STD_LOGIC;

Rst : in STD_LOGIC;

En : in Std_logic;

State_output : out STD_LOGIC_VECTOR (3 downto 0));

end COMPONENT;

COMPONENT MUX32x8 is

Port (INPUT : in STD_LOGIC_VECTOR (31 downto 0);

control : in STD_LOGIC_VECTOR(1 downto 0);

OUTPUT : out STD_LOGIC_VECTOR (7 downto 0));

end COMPONENT;

COMPONENT Decoder is

Port (E : in STD_LOGIC;

F : in STD_LOGIC;

OV : in STD_LOGIC;

```

        A:in std_logic;

        S:in std_logic;

        overflowAr:in std_logic;

        U:in std_logic;

        SWAP:in std_logic;

        Mode0:in std_logic;

        Mode1:in std_logic;

        Mode2:in std_logic;

segmentLED : out STD_LOGIC_VECTOR (31 downto 0));

end COMPONENT;

```

COMPONENT Coder is

```

Port ( Input : in STD_LOGIC_VECTOR (3 downto 0);

Output : out STD_LOGIC_VECTOR (1 downto 0));

end COMPONENT;

```

begin

count: BehCounter

```

    PORT MAP (Clk => Clk,

               Rst => Rst,

               Q => CounterPipe);

```

TheFSM: SSDFSM

```

    PORT MAP (Clk => Clk,

               Rst => Rst,

```

```
En => CounterPipe,  
State_output => FSMOutPipe);
```

Mux: MUX32x8

```
PORT MAP(INPUT => muxInPipe,  
          control=>muxControl,  
          OUTPUT => SSControl);
```

myDecoder: Decoder

```
PORT MAP(E => Empty,  
          F => Full,  
          OV => Stack_OVF,  
          A=>A,  
          S=>S,  
          U=>U,  
          overflowAr=>overflowAr,  
          SWAP=>SWAP,  
          Mode0=>Mode0,  
          Mode1=>Mode1,  
          Mode2=>Mode2,  
          segmentLED => muxInPipe);
```

myCoder: Coder

```
PORT MAP(Input => FSMOutPipe,  
          Output => muxControl);
```

```
ANControl <= FSMOutPipe;
```

```
end Behavioral;
```

COMPARATOR

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity Comparator_Equality is
```

```
Port ( B1 : in  STD_LOGIC_VECTOR (4 downto 0);
```

```
      B2 : in  STD_LOGIC_VECTOR (4 downto 0);
```

```
      Y1 : out STD_LOGIC);
```

```
end Comparator_Equality;
```

```
architecture Behavioral of Comparator_Equality is
```

```
signal xnout0,xnout1,xnout2,xnout3,xnout4:std_logic;
```

```
signal andout0,andout1,andout2,equal_out:std_logic;
```

```
component xnor_gate is
```

```
Port ( B1 : in  STD_LOGIC;
```

```
      B2 : in  STD_LOGIC;
```

```
      Y1 : out STD_LOGIC);
```

```
end component;
```

```
component and_gate is
```

```
Port ( B1 : in  STD_LOGIC;
```

```
B2 : in STD_LOGIC;  
Y1 : out STD_LOGIC);  
end component;
```

```
begin  
  
gate_xnor0: xnor_gate PORT MAP(B1=>B1(0),B2=>B2(0),Y1=>xnout0);  
gate_xnor1: xnor_gate PORT MAP(B1=>B1(1),B2=>B2(1),Y1=>xnout1);  
gate_xnor2: xnor_gate PORT MAP(B1=>B1(2),B2=>B2(2),Y1=>xnout2);  
gate_xnor3: xnor_gate PORT MAP(B1=>B1(3),B2=>B2(3),Y1=>xnout3);  
gate_xnor4: xnor_gate PORT MAP(B1=>B1(4),B2=>B2(4),Y1=>xnout4);  
  
gate_and0 : and_gate PORT MAP(B1=>xnout0,B2=>xnout1,Y1=>andout0);  
gate_and2 : and_gate PORT MAP(B1=>andout0,B2=>xnout2,Y1=>andout1);  
gate_and3 : and_gate PORT MAP(B1=>andout1,B2=>xnout3,Y1=>andout2);  
gate_and4 : and_gate PORT MAP(B1=>andout2,B2=>xnout4,Y1=>equal_out);  
  
Y1<=equal_out;  
  
end Behavioral;
```